

Find Z_L, P_L such that P_L is maximized.

What if Z_L is resistive only?

① First we will do a Thevenin analysis to find Z_{Th}


$$Z_{Th} = 10 \parallel -j5 \parallel j20 = \frac{1}{\frac{1}{10} + \frac{1}{j20} - \frac{1}{j5}} = \frac{1}{\frac{2j + 1 - 4}{j20}} = \frac{j20}{2j - 3}$$

$$= \frac{40}{13} - j\frac{60}{13} \approx 5.55 \angle -56.3^\circ \Omega$$

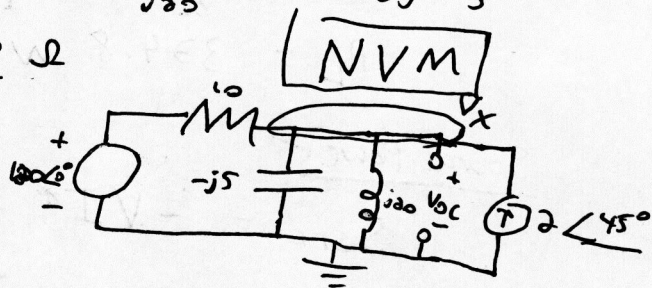B) node voltage method:

$$\frac{V_x - 120}{10} - \frac{V_x}{j5} + \frac{V_x}{j20} - 20 \angle 45^\circ = 0$$

$$V_x \left[\frac{1}{10} - \frac{1}{j5} + \frac{1}{j20} \right] = 12 + 20 \angle 45^\circ \quad \therefore V_{oc} = V_x = 74.8 \angle -50.3^\circ \text{ V (rms)}$$




② Ideal case

$$X_L = -X_{Th}$$

$$R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$$

$$\text{So } Z_L = \frac{40}{13} + j\frac{60}{13} \Omega$$

Reforming our Thevenin Equivalent:

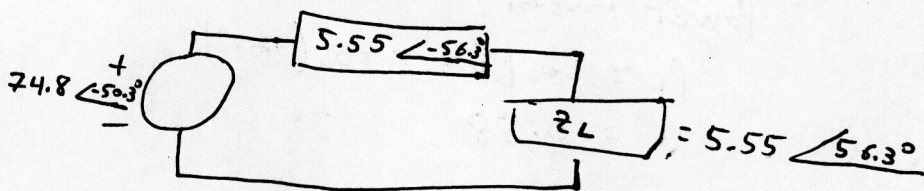

$$I = \frac{V_{oc}}{Z_{eq}} = \frac{V_{oc}}{Z_{Th} + Z_L} = \frac{V_{oc}}{\frac{40}{13} - j\frac{60}{13} + \frac{40}{13} + j\frac{60}{13}} = \frac{V_{oc}}{\frac{80}{13}} = (74.8) \left(\frac{13}{80} \right) \angle -50.3^\circ$$

$$= 12.15 \angle -50.3^\circ \text{ A (rms)}$$

Load Power

$$S_L = V_L I_L^* = I_L Z_L I_L^* = [12.15][12.15][5.55] \angle 50.3 - 50.3 + 56.3^\circ$$

$$= 867 \angle 56.3^\circ \text{ VA}$$

$$P_L = 867 \cos 56.3^\circ = 478.6 \text{ W}$$

Note since our load impedance (overall) is balanced, we have a unity power factor at the source

$$Z_{eq} = \frac{80}{13} \Omega \quad S_{src} = (-74.8 \angle -50.3^\circ)(12.15 \angle -50.3^\circ)^* = -957 \text{ VA}$$

$$P_L = -957 \text{ W}$$

② Non-Ideal

Since $X_L = 0$, $R_L = \sqrt{R_{Th}^2 + (0 + X_{Th})^2} = \sqrt{\left(\frac{40}{13}\right)^2 + \left(\frac{-60}{13}\right)^2} = 5.55 \Omega$

$Z_L = 5.55 \angle 0^\circ \Omega$

$$I = \frac{V_{oc}}{Z_{Th} + Z_L} = \frac{V_{oc}}{\cancel{8.78} 5.55 + \frac{40}{13} + \frac{-j60}{13}} = \frac{74.8 \angle -50.3^\circ}{9.78 \angle -28^\circ} \Omega$$

$$= 7.65 \angle -22^\circ$$

Load Power

$$S = \left(5.55 \angle 0^\circ\right) \left(7.65 \angle -22^\circ\right) \left(7.65 \angle 22^\circ\right) = 324.8 \angle 0^\circ \text{ VA}$$

$P_L = 324.8 \text{ W}$ [All real power]

Source Power

$$S_{src} = -VI^* = -\left(74.8 \angle -50.3^\circ\right) \left(7.65 \angle 22^\circ\right)$$

$$= -572 \angle -28^\circ \text{ VA}$$

$$= -504 + j271.3 \text{ VA}$$


$P_{src} = -504 \text{ W}$

$Q_{src} = 271 \text{ Vars}$

Power Factor

$$PF = \cos(\theta_z) = \cos(-28^\circ)$$

$$= 0.88$$

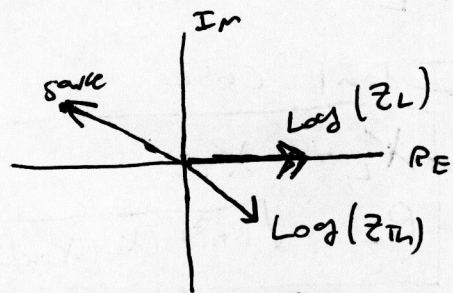

$$S_{Th} = \left(7.65 \angle 0^\circ\right) \left(5.55 \angle -56.3^\circ\right)$$

$$= 180 - 270j \text{ VA}$$

Since $Q_{src} > 0$

and the load is capacitive ($X_L + X_{Th} < 0$)

the ^{load} power is leading.

Capacitive Load \Leftrightarrow Leading Load

Inductive Load \Leftrightarrow Lagging Load