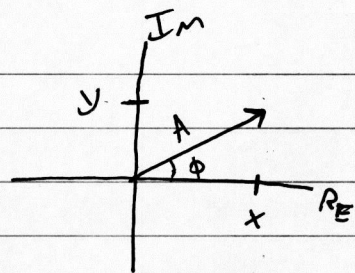


Complex Numbers

$x + jy$ where x is real component
 y is imag component



Polar Form $A \angle \phi = A e^{j\phi}$

Euler's Formula Links these forms

$$A e^{j\phi} = A \cos \phi + j A \sin \phi$$

Conversion: $A = \sqrt{x^2 + y^2}$ $\phi = \tan^{-1}\left(\frac{y}{x}\right)$

General AC Steady State Steps

1) Convert components to phasor form

$\text{---} \text{M} \text{---}$ $R \rightarrow R$

$\text{---} | \text{---}$ $C \rightarrow \frac{-j}{\omega C}$

$\text{---} \text{m} \text{---}$ $L \rightarrow j\omega L$

$A \cos(\omega t + \phi) \rightarrow A \angle \phi$

$A \sin(\omega t + \phi) \rightarrow A \angle \phi - 90^\circ$

2) Solve circuit using phasor form

3) Convert back to time domain

$$A \angle \phi \rightarrow A \cos(\omega t + \phi)$$

$$W = 1000, 50$$


$$2\cos(1000t + 45^\circ) \rightarrow 2 \angle 45^\circ \text{ A}$$

$$40\Omega \rightarrow 40\Omega$$

$$5s \cdot \sin(1000t + 90^\circ) \rightarrow 5 \angle 0^\circ \text{ V}$$

$$50\text{mH} \rightarrow j50$$


$$10\text{mF} \rightarrow -100j$$

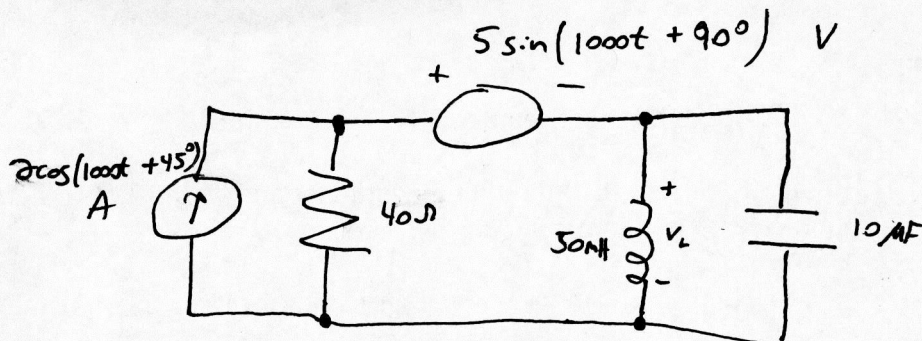

Find $V_L(t)$

~~Node~~ Node Voltage Method:

A and B form a supernode

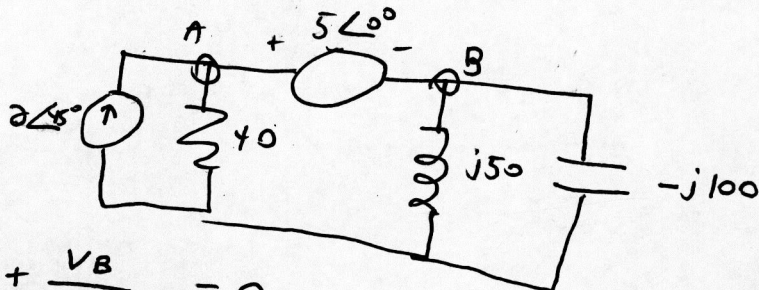

$$\boxed{SN} \quad -2 \angle 45^\circ \text{ A} + \frac{V_A}{40\Omega} + \frac{V_B}{j50} + \frac{V_B}{-100j} = 0$$

$$-2 \angle 45^\circ + \frac{V_A}{40} + V_B \left[\frac{-j}{50} + \frac{j}{100} \right] = 0$$

$$\boxed{NUM} \quad -V_A + 5 + V_B = 0$$

$$V_B = \left[\frac{-j}{100} \right] = 2 \angle 45^\circ \cdot -\frac{V_A}{40}$$

$$V_A = 40 \left[2 \angle 45^\circ + \frac{j}{100} V_B \right]$$

Note that $V_A = V_B + 5$ from \boxed{NUM}

$$V_B + 5 = 40 \left[2\cos 45^\circ + 2j\sin 45^\circ + \frac{j}{100} V_B \right]$$

$$V_B = -5 + 56.6 + j56.6 + j0.4 V_B$$

$$V_B [1 - 0.4j] = 51.6 + j56.6$$

$$V_B [1.08 \angle -21.8^\circ] = 76.6 \angle 47.6^\circ$$

$$\therefore V_B = \frac{76.6}{1.08} \angle 47.6^\circ - (-21.8^\circ) = 70.9 \angle 69.4^\circ$$

$$V_B(t) = 70.9 \cos(1000t + 69.4^\circ)$$